



CS3120

Introduction of Integrated Circuit Design



Chap 7

Electronic Analysis of CMOS Logic Gates

Andy, Yu-Guang Chen

Associate Professor, Department of EE, National Central University

Adjunct Assistant Professor, Department of CS, National Tsing Hua University

andyygchen@ee.ncu.edu.tw



Andy Yu-Guang Chen

1



Outline



- ◆ 7.1 DC Characteristics of the CMOS Inverter
- ◆ 7.2 Inverter Switching Characteristics
- ◆ 7.3 Power Dissipation
- ◆ 7.4 DC Characteristics: NAND and NOR Gates
- ◆ 7.5 NAND and NOR Transient Response
- ◆ 7.6 Analysis of Complex Logic Gates
- ◆ 7.7 Gate Design for Transient Performance
- ◆ 7.8 Transmission Gates and Pass Transistors



Andy Yu-Guang Chen

2

Key Ideas


- ◆ In the previous chapter we examined the electrical characteristics of MOSFETs
- ◆ This sets the foundation for analyzing the behavior of transistors in CMOS logic circuits in this chapter
- ◆ The treatment centers on the important areas of switching speed and layout design, and provides the foundation for much of modern chip design

Andy Yu-Guang Chen

3

 7.1 DC Characteristics of CMOS INV

- ◆ The CMOS inverter gives the basis for calculating the electrical characteristics of logic gates



- ◆ Two types of calculations
 - DC analysis
 - determines V_{out} for a given value of V_{in}
 - Assume V_{in} changes slowly and V_{out} is allowed to stabilize before measurement
 - provides a direct mapping of the input to the output
 - tells us the voltage ranges that define Boolean logic 0 and logic 1 values
 - transient analysis
 - the input voltage is an explicit function of time $V_{in}(t)$
 - the response of the circuit is contained in $V_{out}(t)$
 - the delay between change in the input and the corresponding change at the output
fundamental limiting factor for high-speed design
- ◆ In this section we concentrate on the DC analysis

Andy Yu-Guang Chen


4



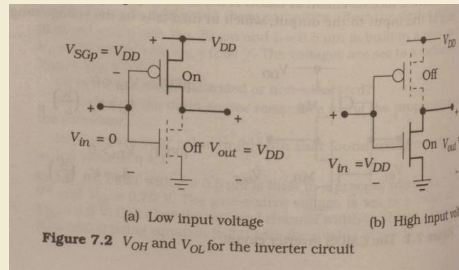7.1 DC Characteristics of CMOS INV



- ◆ Voltage Transfer Characteristic (VTC)
- ◆ VTC is a plot of V_{out} as a function of V_{in}
- ◆ Voltage
 - Output high voltage $V_{OH} = V_{DD}$
 - Output low voltage $V_{OL} = 0V$
- ◆ Logic switching
 - $V_L = V_{OH} - V_{OL} = V_{DD}$
 - Full-rail output



Andy Yu-Guang Chen


5



7.1 DC Characteristics of CMOS INV



- ◆ Voltages
 - $V_{GSn} = V_{in}$
 - $V_{SGp} = V_{DD} - V_{in}$
- ◆ Increasing V_{in}
 - downward transition in the VIC
 - turns the nFET on and the pFET is still conducting
 - Mp goes into cutoff when $V_{in} = V_{DD} - |V_{Tp}|$

 

Andy Yu-Guang Chen

6



7.1 DC Characteristics of CMOS INV



- ◆ The logic 0 and 1 voltage ranges are defined by the changing slope of the VTC
- ◆ Looking for slope = -1
 - Point *a* : input low voltage V_{IL}
 - Logic input 0 is defined as $0 \leq V_{in} \leq V_{IL}$
 - Point *b* : input high voltage V_{IH}
 - Logic input 1 is defined as $V_{IH} \leq V_{in} \leq V_{DD}$

◆ Voltage noise margin

- Give a quantitative measure
- High state: $VNM_H = V_{OH} - V_{IH}$
- Low state: $VNM_L = V_{IL} - V_{OL}$
- Midpoint voltage
 - $V_M = V_{in} = V_{out}$
 - $I_{Dn} = I_{Dp}$

 


Figure 7.3 Voltage transfer curve for the NOT gate

- transition region does not represent a Boolean quantity



Andy Yu-Guang Chen

7



7.1 DC Characteristics of CMOS INV



- ◆ We need to find the operating region (saturation or non-saturation) each FET before we can use the expression
- ◆ Saturation of nFET
 - $V_{sat} = V_{GSn} - V_{Tn} = V_M - V_{Tn}$ (where $V_{in} = V_{GSn} = V_M$)
 - $V_{DSn} = V_{out} = V_M$
 - $V_{DSn} > V_{sat} = V_M - V_{Tn} \rightarrow$ Saturated
- ◆ Current calculation
 - $I_{Dn} = \frac{\beta_n}{2} (V_M - V_{Tn})^2 = \frac{\beta_p}{2} (V_{DD} - V_M - |V_{Tp}|)^2 = I_{Dp}$
 - $\sqrt{\frac{\beta_n}{\beta_p}} (V_M - V_{Tn}) = V_{DD} - V_M - |V_{Tp}|$
 - $V_M = \frac{V_{DD} - |V_{Tp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$
- ◆ V_M is set by nFET-to-pFET ratio
 - $\frac{\beta_n}{\beta_p} = \frac{k'_n (W/L)_n}{k'_p (W/L)_p}$
 - Mobility ratio $\frac{k'_n}{k'_p} = \frac{\mu_n}{\mu_p} = r (\approx 2 \text{ to } 3)$

 


Figure 7.4 Inverter voltages for V_M calculation



Andy Yu-Guang Chen

8



7.1 DC Characteristics of CMOS INV



◆ Symmetric interval

- Equal '0' and '1' input voltage range
- By choosing $V_M = \frac{1}{2} V_{DD}$
- Requires $\beta_n = \beta_p$

◆ Design equation

- $I_{Dn} = \frac{\beta_n}{2} (V_M - V_{Tn})^2 = \frac{\beta_p}{2} (V_{DD} - V_M - |V_{Tp}|)^2 = I_{Dp}$
- $\frac{\beta_n}{\beta_p} = \left(\frac{\frac{1}{2}V_{DD} - |V_{Tp}|}{\frac{1}{2}V_{DD} - V_{Tn}} \right)^2$

◆ PMOS size has 2 to 3 times NMOS size

◆ The choice of transistor size for a particular V_M



Andy Yu-Guang Chen

9



Example 7.1



◆ Consider a CMOS process with the following parameters

- $K'_n = 140 \mu A/V^2$ $V_{Tn} = 0.7$,
- $K'_p = 60 \mu A/V^2$ $V_{Tp} = -0.7V$
- $V_{dd} = 3.0V$

◆ Consider the case where $\beta_n = \beta_p$

◆ A symmetrical design by calculating

- $V_M = \frac{1}{2} V_{DD} = 1.5V = \frac{3-0.7+\sqrt{1}(0.7)}{1+\sqrt{1}}$
- $\frac{\beta_n}{\beta_p} = \frac{k'_n \left(\frac{W}{L}\right)_n}{k'_p \left(\frac{W}{L}\right)_p} = 1$
- $\left(\frac{W}{L}\right)_p = \frac{k'_n}{k'_p} \left(\frac{W}{L}\right)_n = \left(\frac{140}{60}\right) \left(\frac{W}{L}\right)_n = 2.33 \left(\frac{W}{L}\right)_n$

◆ If $\left(\frac{W}{L}\right)_p = \left(\frac{W}{L}\right)_n$

- $V_M = \frac{3-0.7+\sqrt{2.33}(0.7)}{1+\sqrt{2.33}} = 1.33V$



Andy Yu-Guang Chen

10

7.1 DC Characteristics of CMOS INV

- ◆ Figure 7.5 illustrates the difference that uses the two design styles

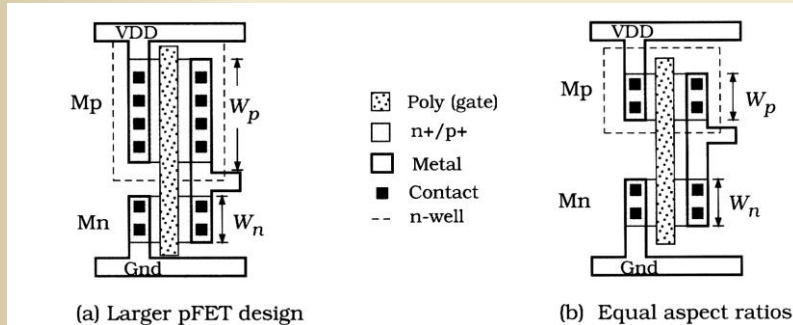


Figure 7.5 Comparison of the layouts for Example 7.1

Andy Yu-Guang Chen

11

7.1 DC Characteristics of CMOS INV

- ◆ At physical level, the relative device sizes contained in the ratio $(\frac{\beta_n}{\beta_p})$ determine the switching point
- ◆ $(\frac{\beta_n}{\beta_p})$ decrease $\Rightarrow V_M$ increases

 


Figure 7.6 Dependence of V_M on the device ratio

Andy Yu-Guang Chen

12

7.2 INV Switching Characteristics

- ◆ High speed digital system design is based on the ability to perform calculation very quickly
 - Logic gates introduce a minimum amount of time delay when input changes
 - Designing fast logic circuit is a more challenging (but critical) aspect of VLSI design
- ◆ Rise and fall time delays
 - Due to the parasitic resistance and capacitances

 


Figure 7.7 General switching waveforms
Andy Yu-Guang Chen

13

7.2 INV Switching Characteristics

- ◆ A simplified RC model in Fig 7.8b
 - $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tn})}$
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$
 - $C_{Dn} = C_{GSn} + C_{DBn} = \frac{1}{2} C_{ox} L' W_n + C_{jn} A_n + C_{jsw n} P_n$
 - $C_{Dp} = C_{GSp} + C_{DBp} = \frac{1}{2} C_{ox} L' W_p + C_{jp} A_p + C_{jsw p} P_p$
- ◆ Increase channel width of a FET increases the parasitic capacitance values

 


Figure 7.8 RC switch model equivalent for the CMOS inverter

Andy Yu-Guang Chen

14

7.2 INV Switching Characteristics

- ◆ In a logic chain, every logic gate must drive another gate, or set of gates, to be useful
- ◆ Fan-out (FO) gates act as load to the driving circuits because of their input capacitance C_{in}
 - $C_{in} = C_{GP} + C_{Gn}$
- ◆ External load capacitance
 - FO = 3
 - $C_L = 3C_{in} = 3 * (C_{GP} + C_{Gn})$

 


Figure 7.9 Input capacitance and load effects

Andy Yu-Guang Chen

15

7.2 INV Switching Characteristics

- ◆ We may now calculate the switching times of the inverter
- ◆ A CMOS NOT gate is used to drive an external load capacity C_L
 - $C_{out} = C_{FET} + C_L$
 - $C_{FET} = C_{Dn} + C_{Dp}$
 - C_{out} is the load the gate must drive

 


Figure 7.10 Evolution of the inverter switching model

Andy Yu-Guang Chen

16

Example 7.2

- ◆ Apply this analysis to find capacitances in the NOT gate

 


Figure 7.11 Example of capacitance calculations

Andy Yu-Guang Chen

17

Example 7.2

- ◆ $C_{Gn} = 2.7 * 1 * 4 = 10.8 \text{ fF}$
- ◆ $C_{GDn} = \frac{1}{2} * 10.8 = 5.04 \text{ fF}$
- ◆ $C_{DBn} = 0.86 * 4 * 2.1 + 0.24 * 2 * (4 + 2.1) = 10.15 \text{ fF}$
- ◆ $C_{Dn} = 5.04 + 10.15 = 15.55 \text{ fF}$
- ◆ $C_{GP} = 2.7 * 1 * 8 = 21.6 \text{ fF}$
- ◆ $C_{GDP} = \frac{1}{2} * 21.6 = 10.8 \text{ fF}$
- ◆ $C_{DBP} = 1.05 * 8 * 2.1 + 0.32 * 2 * (8 + 2.1) = 24.10 \text{ fF}$
- ◆ $C_{DP} = 10.8 + 24.1 = 34.9 \text{ fF}$
- ◆ $C_{FET} = C_{Dp} + C_{Dn} = 15.55 + 34.9 = 50.45 \text{ fF}$
- ◆ $C_{out} = 50.45 + C_L$

Andy Yu-Guang Chen

18

7.2.1 Fall time Calculation

◆ Calculating output fall time t_f

- V_{in} changes from 0 to V_{DD}
- The nFET switch is closed and the pFET switch is open

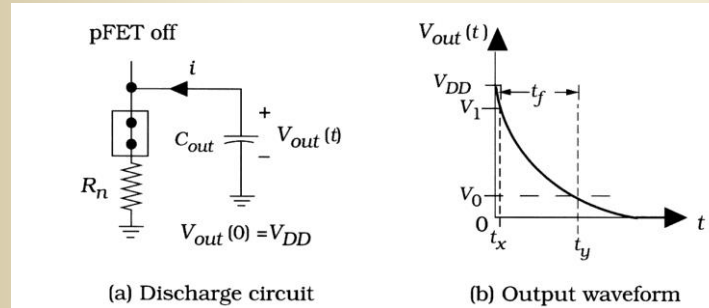


Figure 7.12 Discharge circuit for the fall time calculation

Andy Yu-Guang Chen

19

7.2.1 Fall time Calculation

- ◆ The capacitor C_{out} is initially charged to V_{DD} and is discharged to 0 V.
- ◆ The fall time is traditionally defined to be the time interval
 - $V_1 = 0.9V_{DD}$ to $V_0 = 0.1V_{DD}$
- ◆ Fall time calculation
 - $I = -C_{out}(dV_{out}/dt) = V_{out}/R_n$ (The current leaving the capacitor)
 - $V_{out}(t) = V_{DD}e^{-t/\tau_n}$ (initial condition $V_{out}(0) = V_{DD}$)
 - time constant $\tau_n = R_n C_{out}$
 - $t = \tau_n \ln\left(\frac{V_{DD}}{V_{out}}\right)$
 - $t_f = t_y - t_x = \tau_n \ln\left(\frac{V_{DD}}{0.1V_{DD}}\right) - \tau_n \ln\left(\frac{V_{DD}}{0.9V_{DD}}\right) = \tau_n \ln(9)$
 - $\ln(a) - \ln(b) = \ln\left(\frac{a}{b}\right)$
 - $t_f = t_{HL} = \ln(9) \tau_n \approx 2.2\tau_n = 2.2R_n C_{out}$
 - t_{HL} : high-to-low time

 


Figure 7.12 Discharge circuit for the fall time calculation

Andy Yu-Guang Chen

20

7.2.2 Rise Time Calculation

◆ Calculating output rising time t_r

- V_{in} changes from V_{DD} to 0
- The pFET switch is closed and the nFET switch is open

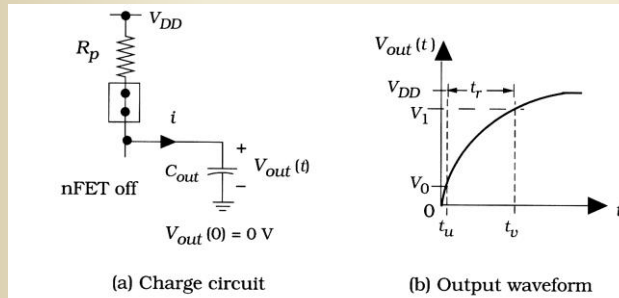


Figure 7.13 Rise time calculation

Andy Yu-Guang Chen

21

7.2.2 rise time Calculation

- ◆ The capacitor C_{out} is initially 0 V and is charged to V_{DD}
- ◆ The rise time is traditionally defined to be the time interval
 - $V_0 = 0.1V_{DD}$ to $V_1 = 0.9V_{DD}$
- ◆ Fall time calculation
 - $I = C_{out} \left(\frac{dV_{out}}{dt} \right) = (V_{DD} - V_{out})/R_p$ (The current going into the capacitor)
 - $V_{out}(t) = V_{DD} [1 - e^{-t/\tau_p}]$ (initial condition $V_{out}(0) = 0V$)
 - time constant $\tau_p = R_p C_{out}$
 - $t_r = t_v - t_u = \tau_p \ln(9)$
 - $t_r = t_{LH} = \ln(9) \tau_p \approx 2.2\tau_p = 2.2R_p C_{out}$
 - t_{HL} : low-to-high time
- ◆ Maximum signal frequency
 - $F_{max} = 1/(t_r + t_f)$

 


Figure 7.13 Rise time calculation

Andy Yu-Guang Chen

22

Example 7.3

- ◆ Consider an inverter circuit that has FET aspect ratios

$$\triangleright \left(\frac{W}{L}\right)_n = 6, \left(\frac{W}{L}\right)_p = 8$$

- ◆ Process

$$\begin{aligned} \triangleright k'_n &= 150 \mu\text{A}/\text{V}^2, V_{Tn} = +0.70 \text{ V} \\ \triangleright k'_p &= 62 \mu\text{A}/\text{V}^2, V_{Tp} = -0.85 \text{ V} \\ \triangleright V_{DD} &= 3.3 \text{ V} \\ \triangleright C_{out} &= 150 \text{ fF} \end{aligned}$$

- ◆ Compute the rise and fall time

$$\begin{aligned} \triangleright R_p &= 1 / [(62 \times 10^{-6})(8)(3.3 - 0.85)] = 822.9 \Omega \\ \triangleright \tau_p &= 822.9 \times 150 \times 10^{-15} = 123.43 \text{ ps} \\ \triangleright t_r &= 2.2 \tau_p = 271.55 \text{ ps} \\ \triangleright R_n &= 427.35 \Omega \\ \triangleright \tau_n &= 64.1 \text{ ps} \\ \triangleright t_f &= 2.2 \tau_n = 141.0 \text{ ps} \end{aligned}$$

- ◆ Compute maximum signal frequency

$$\triangleright f_{max} = \frac{1}{t_r + t_f} = \frac{1}{(271.55 + 141.0) \times 10^{-12}} = 2.45 \text{ GHz}$$

Andy Yu-Guang Chen

23

7.2.3 Propagation Delay

- ◆ The propagation delay is used to estimate the reaction delay time from input to output

- $$\triangleright t_p = \frac{(t_{pf} + t_{pr})}{2}$$
- $\triangleright T_{pf}^{(V_{DD}/2)}$ is the output fall time from the maximum level to the 50% voltage line
 - $\triangleright T_{pr}$ is the output rise time from the 0V to the 50% voltage line ($V_{DD}/2$)
 - \triangleright Using the exponential equations for V_{out}
 - $t_{pf} = \ln(2) \tau_n$
 - $t_{pr} = \ln(2) \tau_p$
 - $\ln(2) \approx 0.693$
 - $t_p \approx 0.35(\tau_n + \tau_p)$

 


Figure 7.14 Propagation time definitions

- ◆ Propagation delay are commonly used in basic logic simulation


- \triangleright Not provide details on rise and fall time

Andy Yu-Guang Chen

24

Delay Definitions

- ◆ t_{pdr} : rising propagation delay
 - From input to rising output crossing $V_{DD}/2$
- ◆ t_{pdf} : falling propagation delay
 - From input to falling output crossing $V_{DD}/2$
- ◆ t_{pd} : average propagation delay
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- ◆ t_r : rise time
 - From output crossing $0.1 V_{DD}$ to $0.9 V_{DD}$
- ◆ t_f : fall time
 - From output crossing $0.9 V_{DD}$ to $0.1 V_{DD}$

 


5: DC and Transient Response

Andy Yu-Guang Chen

25

Simulated Inverter Delay

 - ◆ Solving differential equations by hand is too hard
- ◆ SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- ◆ But simulations take time to run, may hide insight




5: DC and Transient Response

Andy Yu-Guang Chen

26

7.2.4 General Analysis

- ◆ We should know how to design single logic gates and then characterize the behavior of the gates when they are cascaded
- ◆ Total output capacitance
 - $C_{out} = C_{FET} + C_L$
 - The layout geometry establishes the value of C_{FET}
 - C_L varies with the application
- ◆ Rise and fall time
 - $t_r \approx 2.2R_p(C_{FET} + C_L) = t_{r0} + \alpha_p C_L$
 - $t_f \approx 2.2R_n(C_{FET} + C_L) = t_{f0} + \alpha_n C_L$
 - Rise and fall time are linear functions of C_L
 - $\alpha_p = 2.2R_p = \frac{2.2}{\beta_p(V_{DD} - |V_{Tp}|)}$
 - $\alpha_n = 2.2R_n = \frac{2.2}{\beta_p(V_{DD} - V_{Tn})}$
 - Inversely proportional to the aspect ratios
 - Under zero-load condition ($C_L = 0$)
 - $t_r = t_{r0} \approx 2.2R_p C_{FET}$
 - $t_f = t_{f0} \approx 2.2R_n C_{FET}$
- ◆ Large capacitive loads may cause problems because of longer delays
- ◆ t_r and t_f can be reduced by using large FETs

 

Andy Yu-Guang Chen

27

Example 7.4

- ◆ Use the results of Example 7.3 to find the general delay equations when $C_{FET} = 80fF$
- ◆ t_r is controlled by the pFET
 - $R_p = 822.9\Omega$
 - $\alpha_p = 2.2R_p = 1810.4\Omega$
 - $t_{r0} = 2.2R_p C_{FET} = 2.2(822.9)(80 \times 10^{-15}) = 144.9 ps$
 - $t_r = t_{r0} + \alpha_p C_L = 144.9 + 1.810C_L ps$
- ◆ t_f is controlled by the nFET
 - $R_n = 427.35\Omega$
 - $\alpha_n = 2.2R_p = 940.2\Omega$
 - $t_{f0} = 2.2R_n C_{FET} = 2.2(940.2)(80 \times 10^{-15}) = 165.5 ps$
 - $t_f = t_{f0} + \alpha_n C_L = 165.5 + 0.940C_L ps$
- ◆ Assume $C_L = 150 fF$
 - $t_r = 144.9 + 1.810(150) = 416.4 ps$
 - $t_f = 165.5 + 0.940(150) = 306.5 ps$
 - Maximum signal frequency $= f_{max} = \frac{1}{t_r + t_f} = 1.38GHz$

Andy Yu-Guang Chen

28

7.2.5 Summary of Inverter

- ◆ Electrical characteristics are established by
 - The processing variables: k' , V_T , and parasitic capacitances
 - The transistor aspect ratios $\left(\frac{W}{L}\right)_n$ and $\left(\frac{W}{L}\right)_p$
- ◆ VLSI designers do not have control over processing parameters
- ◆ Device sizing becomes the critical issue

Andy Yu-Guang Chen

29

7.3 Power Dissipation

- ◆ The current I_{DD} flowing from power supply to ground gives a dissipated power $P = V_{DD}I_{DD}$
- ◆ Current can be divided into DC and dynamic (or switching) contributions $P = P_{DC} + P_{dyn}$
- ◆ Ideally, the DC current is 0 when $V_{in} = 0$
 - Quiescent leakage current I_{DDQ}
 - DC power at stable 0 or 1 state
 - $P_{DC} = V_{DD}I_{DDQ}$

 
 


Figure 7.17 DC current flow

Andy Yu-Guang Chen

30

7.3 Power Dissipation

◆ Dynamic power dissipation

➤ A complete cycle effectively creates a path for current to flow from the power supply to ground

➤ Discharge

- $Q_e = C_{out}V_{DD}$
- $P_{av} = V_{DD}I_{DD} = V_{DD} \left(\frac{Q_e}{T} \right)$: average power dissipated over a single cycle T
- $P_{sw} = C_{out}V_{DD}^2f$
- The dynamic power is proportional to the signal frequency

$$◆ P = P_{DC} + P_{dyn} = V_{DD}I_{DDQ} + C_{out}V_{DD}^2f$$

 


Figure 7.18 Circuit for finding the transient power dissipation

31

7.4 DC Characteristics: NAND and NOR

7.4.1 NAND Analysis

◆ In this section we will examine the relationship between device sizes and transitions described by the VTC

◆ NAND2

➤ Like-polarity FETs have the same aspect ratio: β_n and β_p

 


Figure 7.20 NAND2 VTC analysis

Andy Yu-Guang Chen

 


Figure 7.19 NAND2 logic circuit

32

7.4.1 NAND Analysis

- ◆ Calculate the value of midpoint voltage V_M for the case of simultaneous switching

 


Figure 7.21 Layout of NAND2 for V_M calculation

Andy Yu-Guang Chen

33

7.4.1 NAND Analysis

- ◆ “Merge” the two gates together into one
- ◆ nFET
 - The structure can be approximated as a single nFET with an aspect ratio of $(\frac{W_n}{2L})$
 - single equivalent transistor is described by the value $\frac{\beta_n}{2}$
- ◆ pFET
 - The structure can be simplified into the single gate with an aspect ratio of $(\frac{2W_p}{L})$
 - single equivalent transistor is described by the value $2\beta_p$

 


Figure 7.22 Simplification of the series-connected nFETs

 


Figure 7.23 Simplification of parallel-connected pFETs

Andy Yu-Guang Chen

34

7.4.1 NAND Analysis

◆ Find V_M

- Replacing the transistor pairs by their single-FET
- Recall: $I_{Dn} = \frac{\beta_n}{2}(V_M - V_{Tn})^2 = \frac{\beta_p}{2}(V_{DD} - V_M - |V_{Tp}|)^2 = I_{Dp}$
- $\frac{\beta_n}{2}(V_M - V_{Tn})^2 = \frac{2\beta_p}{2}(V_{DD} - V_M - |V_{Tp}|)^2$
- $$V_M = \frac{V_{DD} - |V_{Tp}| + \frac{1}{2}\sqrt{\frac{\beta_n}{\beta_p}}V_{Tn}}{1 + \frac{1}{2}\sqrt{\frac{\beta_n}{\beta_p}}}$$
- The $\frac{1}{2}$ reduces the denominator, which is why the VTC curves shifted toward the right

◆ For N-input NAND gate

$$V_M = \frac{V_{DD} - |V_{Tp}| + \frac{1}{N}\sqrt{\frac{\beta_n}{\beta_p}}V_{Tn}}{1 + \frac{1}{N}\sqrt{\frac{\beta_n}{\beta_p}}}$$

 


Figure 7.20 NAND2 VTC analysis

 


Figure 7.24 Simplified V_M circuit for the NAND2 gate

Andy Yu-Guang Chen

35

7.4.2 NOR Analysis

◆ The NOR2 gate can be analyzed using the same techniques

- $V_{out} = V_{DD}$ requires $V_A = V_B = 0$
- nFET are in parallel: $2\beta_n$
- pFET are in serial: $\frac{\beta_p}{2}$
- $\frac{2\beta_n}{2}(V_M - V_{Tn})^2 = \frac{(\beta_p/2)}{2}(V_{DD} - V_M - |V_{Tp}|)^2$
- $$V_M = \frac{V_{DD} - |V_{Tp}| + 2\sqrt{\frac{\beta_n}{\beta_p}}V_{Tn}}{1 + 2\sqrt{\frac{\beta_n}{\beta_p}}}$$

 


Figure 7.25 NOR2 circuit

◆ the NAND and NOR gates tend have opposite behaviors with respect to the reference NOT gate VTC

 


Figure 7.26 NOR2 VTC construction

 


Figure 7.27 NOR2 V_M calculation for simultaneous switching

Andy Yu-Guang Chen

36



7.4 DC Characteristics: NAND and NOR



- ◆ Both the NAND and NOR gates exhibit low DC power dissipation values
 - $P_{DC} = V_{DD}I_{DDQ}$
 - No direct current flow path from the power supply to ground when the inputs are stable logic 0 or logic 1 values
- ◆ Dynamic power is still present in the general form
 - $P_{sw} = C_{out}V_{DD}^2f_{gate}$
 - f_{gate} is different from the basic Switching frequency used for the inverter



Andy Yu-Guang Chen

37



7.5 NAND and NOR Transient Response



- ◆ Transient switching times often represent the limiting factor in designing a digital logic chain
- ◆ Examine how the FET topology and device sizing affect the operational speed of the gate



Andy Yu-Guang Chen

38

7.5.1 NAND2 Switching Times

- ◆ The transient calculations are based on finding RC time constants
- ◆ We will concentrate estimating the worst-case values of the switching times
 - $C_{out} = C_{FET} + C_L$
 - $C_{FET} = C_{Dn} + 2C_{Dp}$
 - two pFETs are connected to the output node
 - The drawing identifies the transistors by their resistance values
 - $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tn})}$
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$

 


Figure 7.28 NAND2 circuit for transient calculations

Andy Yu-Guang Chen

39

7.5.1 NAND2 Switching Times

- ◆ Rising time t_r
 - If only one pFET is conducting
 - C_{out} charges through a pFET resistance R_p
 - $V_{out}(t) = V_{DD}[1 - e^{-t/\tau_p}]$ (initial condition $V_{out}(0) = 0V$)
 - $t_r = 2.2\tau_p = 2.2R_pC_{out} = t_0 + \alpha_0C_L$
 - $t_0 = 2.2R_pC_{FET}$: zero-load value
 - $\alpha_0 = 2.2R_p$: slope of t_r
 - Best case: both pFET are conducting
 - $R_p/2$

 


Figure 7.29 NAND2 subcircuits for estimating rise and fall times

Andy Yu-Guang Chen

40

7.5.1 NAND2 Switching Times

- ◆ Fall time t_f
 - C_{out} discharges through the series-connected nFET chain
 - RC modeling of each device leads to the “ladder” network
 - Consider the presence of the inter-FET capacitance C_x
 - In worst case, C_x will have charge that will flow through lower nFET (MnA) to ground
 - The discharge rate is limited by the current that MnA can maintain
 - $V_{out}(t) = V_{DD}e^{-t/\tau_n}$
 - Time constant is given by the Elmore formula
 - $\tau_n = \tau_{n1} + \tau_{n2} = C_{out}(R_n + R_n) + C_x R_n$
 - $t_f = 2.2\tau_n = 2.2[(C_{FET} + C_L)(2R_n) + C_x R_n]$
 - $t_f = t_1 + \alpha_1 C_L$
 - $t_1 = 2.2R_n(2C_{FET} + C_x)$: zero-load value
 - $\alpha_1 = 4.4R_n$: slope of t_f
- ◆ Series-connected FETs lead to longer delays in CMOS circuits
 - $\tau_n = R_n(2C_{out} + C_x)$
 - $C_{eff} = 2C_{out} + C_x$

 


Figure 7.29 NAND2 subcircuits for estimating rise and fall times

Andy Yu-Guang Chen

41

7.5.2 NOR2 Switching Times

- ◆ The analysis of the NOR2 transients proceeds in the same manner
- ◆ We will concentrate estimating the worst-case values of the switching times
 - $C_{out} = C_{FET} + C_L$
 - $C_{FET} = 2C_{Dn} + C_{Dp}$
 - two nFETs are connected to the output node
 - The drawing identifies the transistors by their resistance values
 - $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tn})}$
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$

 


Figure 7.30 NOR2 circuit for switching time calculations


Andy Yu-Guang Chen

42

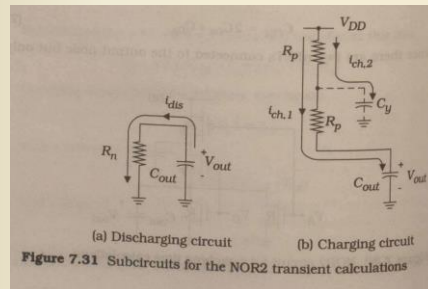7.5.2 NOR2 Switching Times

◆ Fall time t_f

- If only one nFET is conducting
- C_{out} discharges through a nFET resistance R_n
- $V_{out}(t) = V_{DD}e^{-t/\tau_n}$ (initial condition $V_{out}(0) = V_{DD}$)
- $t_f = 2.2\tau_n = 2.2R_nC_{out} = t_1 + \alpha_1C_L$
- $t_1 = 2.2R_nC_{FET}$: zero-load value
- $\alpha_1 = 2.2R_p$: slope of t_f




Andy Yu-Guang Chen

43

 7.5.2 NOR2 Switching Times

◆ Rising time t_r

- C_{out} charges through the series-connected pFET chain
- RC modeling of each device leads to the "ladder" network
- Consider the presence of the inter-FET capacitance C_y
- C_y will be charged during rising event
- $V_{out}(t) = V_{DD}[1 - e^{-t/\tau_p}]$ (initial condition $V_{out}(0) = 0V$)
- Time constant is given by the Elmore formula
 - $\tau_p = \tau_{p1} + \tau_{p2} = C_{out}(R_p + R_p) + C_yR_p$
- $t_r = 2.2\tau_p = 2.2[(C_{FET} + C_L)(2R_p) + C_yR_p]$
- $t_r = t_0 + \alpha_0C_L$
- $t_0 = 2.2R_p(2C_{FET} + C_y)$: zero-load value
- $\alpha_0 = 4.4R_p$: slope of t_r



◆ Series-connected FETs lead to longer delays in CMOS circuits

- $\tau_n = R_n(2C_{out} + C_x)$
- $C_{eff} = 2C_{out} + C_x$

Andy Yu-Guang Chen

44



Elmore Delay




- ◆ ON transistors look like resistors
- ◆ Pullup or pulldown network modeled as *RC ladder*
- ◆ Elmore delay of RC ladder

$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



2024/11/15

 

Andy Yu-Guang Chen

45



7.5.3 Summary



- ◆ The analyses above illustrate that the NAND and NOR gates exhibit complementary characteristics at both the DC and transient levels
- ◆ General statements about NAND and NOR gates as compared to the simpler NOT circuit
 - Rise time
 - $t_r = t_0 + \alpha_0 C_L$
 - Fall time
 - $t_f = t_1 + \alpha_1 C_L$
 - The constants depend upon the parasitic transistor resistances and capacitances
 - Adding complementary transistor pairs increases the delay time because C_{FET} is increased
- ◆ Switching delay increases with the # of fan-ins (FIs)
- ◆ Switching delay increases with the external load



Andy Yu-Guang Chen

46

7.6 Analysis of Complex Gates

- ◆ The analysis techniques developed for the NAND and NOT circuits may be extended to analyze complex CMOS logic gates with AOI and OAI structure
 - series-connected FETs

- ◆ Consider the function $f = \overline{x \cdot (y + z)}$

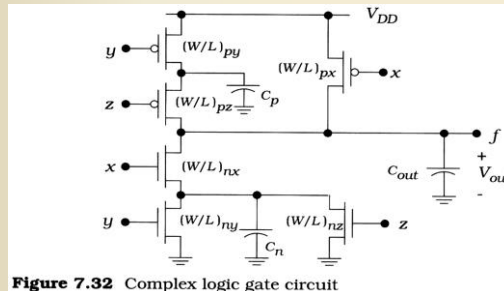


Figure 7.32 Complex logic gate circuit

Andy Yu-Guang Chen

47

7.6 Analysis of Complex Gates

- ◆ Fall time analysis

- Assume they are all the same size $\left(\frac{W}{L}\right)_{nx} = \left(\frac{W}{L}\right)_{ny} = \left(\frac{W}{L}\right)_{nz}$
- Resistance: R_n can be used
- Worst case fall time: $x = 1$, but only one of the ORed inputs y or z is 1
 - 2-FET series pair
 - $C_{out} = C_{FET} + C_L$
 - $\tau_n = R_n C_n + 2R_n C_{out}$
 - $t_f = 2.2\tau_n = 2.2R_n [C_n + 2(C_{FET} + C_L)] = t_1 + \alpha_1 C_L$
 - Zero load time: $t_1 = 2.2R_n (C_n + 2C_{FET})$
 - Slop: $\alpha_1 = 2.2R_n$

Andy Yu-Guang Chen

48



7.6 Analysis of Complex Gates



◆ Rise time analysis

- Assume they are all the same size $\left(\frac{W}{L}\right)_{px} = \left(\frac{W}{L}\right)_{py} = \left(\frac{W}{L}\right)_{pz}$
- Resistance: R_p can be used
- the limiting series chain is with the y and z input p-channel transistors
- the x-input pFET provides the fast switching, and could be decreased to half-size without affecting the result
- The series chain gives
 - $\tau_p = R_p C_p + 2R_p C_{out}$
 - $t_r = t_0 + \alpha_0 C_L$
 - Zero load time: $t_0 = 2.2R_p(C_p + 2C_{FET})$
 - Slope: $\alpha_0 = 2.2R_p$ x 2

◆ An arbitrary gate yields equations of the same form for both the rise fall times, illustrating the generality of the procedure



Andy Yu-Guang Chen

49



7.6.1 Power Dissipation



◆ Power is proportional to the **activity coefficient** α

- which represents the probability that an **output 0->1 transition** takes places during one period.
- $P = V_{dd} I_{DQ} + C_{out} V_{dd}^2 f (P_{dyn})$
- $P_{dyn} = \alpha C_{out} V_{dd}^2 f$

◆ For a network that consists of N gates, the total dynamic power is

- $P_{dyn} = \sum_{i=1}^N \alpha_i C_i V_i V_{DD} f$
 - α_i : activity coefficient
 - C_i : node capacitance that charges to a maximum value of V_i .

◆ Activity coefficients can be determined from truth tables

- $\alpha = p_0 p_1$
- $\alpha_{NOR2} = 3/4 * 1/4 = 3/16$
- $\alpha_{NAND2} = 3/4 * 1/4 = 3/16$
- $\alpha_{NOR3} = 1/8 * 7/8 = 7/64$
- $\alpha_{XOR2} = 1/2 * 1/2 = 1/4$

A	B	$A + B$	$A \cdot B$
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0



Andy Yu-Guang Chen

50



7.7 Gate Design for Transient Performance



- ◆ High-speed circuits are limited by the switching time of individual gates
- ◆ The aspect ratios are the critical design parameters for the DC and transient switching times
- ◆ The DC switching characteristics are often considered less important than the switching speed
- ◆ The design philosophy used to select aspect ratios varies with situation
 - use the inverter as a reference and then attempt to design other gates that have approximately the same switching times



Andy Yu-Guang Chen


51



7.7 Gate Design for Transient Performance



- ◆ device transconductance as being equivalent to the aspect ratio
 - $\beta = k' \left(\frac{W}{L} \right)$
- ◆ In Fig 7.34(a)
 - both transistors drive the same capacitance, the difference is in the resistance values
 - $R_p = \frac{1}{\beta_p(V_{DD} - |V_{Tp}|)}$ $R_n = \frac{1}{\beta_n(V_{DD} - V_{Tn})}$
 - symmetrical inverter: $\beta_p = \beta_n$
 - requires the device sizes: $\left(\frac{W}{L} \right)_p = r \left(\frac{W}{L} \right)_n$
 - Process transconductance ratio: $r = \frac{k'_n}{k'_p}$

 

Andy Yu-Guang Chen

52

7.7 Gate Design for Transient Performance

◆ Find the device sizes β_P and β_N for the NAND2 gate with similar rise and fall times

➤ rise time

- worst situation is where only one transistor contributes to the rise time
- $\beta_P = \beta_p$

➤ fall time

- series-connected nFET chain: two series-connected resistors between the output and ground

$$R = R_N + R_N, R_N = \frac{1}{\beta_N(V_{DD} - V_{TN})}$$

- using the inverter as a reference

$$\begin{aligned} - R &= R_n = 2R_N \\ - \frac{1}{\beta_n(V_{DD} - V_{TN})} &= \frac{2}{\beta_N(V_{DD} - V_{TN})} \\ - \beta_N &= 2\beta_n \end{aligned}$$

- the series-connected nFETs are twice as large as the inverter

$$\left(\frac{W}{L}\right)_N = 2 \left(\frac{W}{L}\right)_n$$

- The resulting fall time will be larger because of the larger output capacitance and the FET-FET internal capacitance

 


Figure 7.34 Relative FET sizing

Andy Yu-Guang Chen

53

7.7 Gate Design for Transient Performance

◆ Find the device sizes β_P and β_N for the NOR2 gate with similar rise and fall times

◆ With the similar idea

➤ fall time


- $\beta_N = \beta_n$

➤ rise time

$$\frac{1}{\beta_P(V_{DD} - |V_{TP}|)} = \frac{2}{\beta_P(V_{DD} - |V_{TP}|)}$$

$$\beta_P = 2\beta_p$$
 
$$\left(\frac{W}{L}\right)_P = 2 \left(\frac{W}{L}\right)_p$$



(c) NOR2

Andy Yu-Guang Chen

54

7.7 Gate Design for Transient Performance

- ◆ This technique can be extended to larger chains.

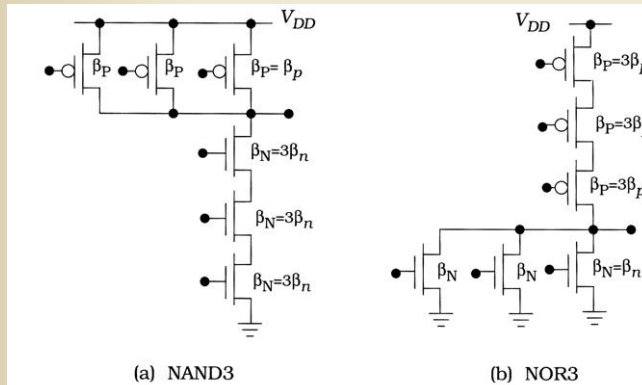


Figure 7.35 Sizing for 3-input gates

Andy Yu-Guang Chen

55

7.7 Gate Design for Transient Performance

- ◆ Complex logic gates can be designed in the same manner

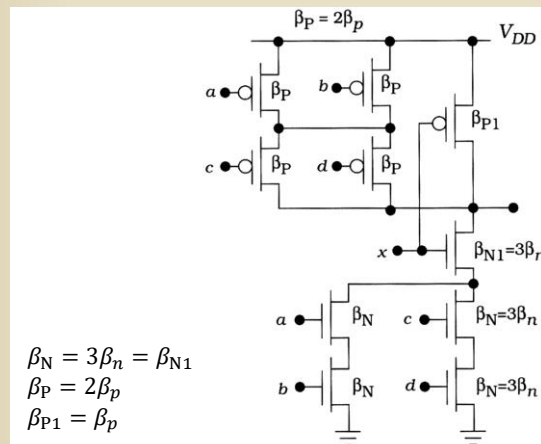


Figure 7.36 Sizing of a complex logic gate

Andy Yu-Guang Chen

56



7.8 Transmission Gates & Pass Transistor



- ◆ Transmission gates consist of an nFET/pFET pair wired in parallel

 


Figure 7.37 Transmission gate modeling

- ◆ Even though the FETs are in parallel, one usually dominates the conduction process at any given time
 - logic 0 transmission is controlled by the nFET
 - $R_{TG} = \max(R_n, R_p)$
 - $C_{in} = C_{S,n} + C_{D,p}$
- ◆ large values of (W/L) decrease the resistance, but a large W implies large capacitances



Andy Yu-Guang Chen

57



7.8 Transmission Gates & Pass Transistor



注重特定方向，另一方向不在乎，差距可達6倍

- ◆ **Pass transistors** are single FETs that pass the signal between the drain and source terminals instead of a fixed power supply value

 


Figure 7.38 nFET pass transistor

 


Figure 7.39 Voltage waveforms for an nFET pass transistor



Andy Yu-Guang Chen

58



Conclusions

- ◆ DC Characteristics of CMOS Inverters and Gates
- ◆ Switching Characteristics and Propagation Delay
- ◆ Power Dissipation
- ◆ Transient Response of NAND and NOR Gates
- ◆ Complex Gate Analysis and Design for Transient Performance
- ◆ Transmission Gates and Pass Transistors



Andy Yu-Guang Chen

59



Q&A



Andy Yu-Guang Chen

60



Andy, Yu-Guang Chen
 Associate Professor, Department of EE, NCU
 Email: andyygchen@ee.ncu.edu.tw
 FB: Yu-Guang Chen
 IG: ncu.eda.andy
 Google account: andyygchen.ncu

Andy Yu-Guang Chen

61