



CS3120

Introduction of Integrated Circuit Design



# Chap 3

## Physical Structure of CMOS Integrated Circuits

Andy, Yu-Guang Chen

Associate Professor, Department of EE, National Central University

Adjunct Assistant Professor, Department of CS, National Tsing Hua University

andygchen@ee.ncu.edu.tw



1



## Outline



- ◆ 3.1 Integrated Circuit Layers
- ◆ 3.2 MOSFETS
- ◆ 3.3 CMOS Layers
- ◆ 3.4 Designing FET Arrays



2



## From Logic To Physical



- ◆ CMOS integrated circuits are electronic switching networks
- ◆ A primary task of VLSI designer is to **translate circuit schematics into silicon form**
- ◆ Physical design separates VLSI from general digital engineering
- ◆ In this chapter, we will examine the **structure** of a CMOS integrated circuit as seen at the microscopic silicon level in the design hierarchy



2024/9/27

Andy Yu-Guang Chen


3



## 3.1 Integrated Circuit Layers



- ◆ A silicon integrated circuit can be viewed as a collection of patterned material layers.
  - Metal (copper, aluminum), insulators (silicon dioxide( $\text{SiO}_2$ ) known as quartz glass), silicon (semiconductor or “partial” conductor)
  - Silicon IC: stacking different layers of materials in a specific order to form three dimensional structures

 

**Figure 3.1** Two separate material layers




4

## 3.1 Integrated Circuit Layers

### ◆ Layers after the stacking process

- VLSI chip: employ several conducting layers of aluminum or copper
- Pattern conducting layers on the top of insulators
- Insulators are often (assumed) omitted from top views ( $\text{SiO}_2$ )

 


**Figure 3.2** Layers after the stacking process is completed

## 3.1 Integrated Circuit Layers

### ◆ Add more layers

- First, coat the surface with another of insulating glass
- To provide a flat surface, do **CMP** (chemical-mechanical planarization)
  - Etched and sanded for a flat surface
- Next, we coat the surface with the second metal layer (M2)
  - Two do not touch

 


**Figure 3.3** Addition of another insulator and a second metal layer



## 3.1 Integrated Circuit Layers

### ◆ Visualize the three-dimensional structure

- The **side view** illustrate the order of the stacking
  - In the manufacturing process
- **Insulating** layers separate the two metals so that they are electrically distinct
- The patterning of each layer is shown by a top view perspective
  - By a VLSI designer

 


**Figure 3.3** Addition of another insulator and a second metal layer

 

## 3.1 Integrated Circuit Layers

### ◆ Visualize the three-dimensional structure



Intel 90 nm Stack

[Thompson02]

Intel 45 nm Stack

[Moon08]



14: Wires

8



## 3.1 Integrated Circuit Layers



- ◆ The stacking order is established in the manufacturing process and can not be altered by the VLSI designer
- ◆ Creating the pattern for each layer is a critical part of the chip design sequence
  - It defines the locations and sizes of all MOSFETs and specifies how the transistors are connected together



2024/9/27

Andy Yu-Guang Chen


9



### 3.1.1 Interconnect Resistance & Capacitance



- ◆ The logic gates communicate each other by wires (interconnects)
- ◆ Signal transfer speed is directly affected physical implementation of the wiring
  - Making it a very important of chip design.
- ◆ Resistance ( $R$ ) measured by Ohm ( $\Omega$ )
  - $V = I \cdot R \rightarrow R = V/I$  (volts/amperes)
- ◆ Parasitic (unwanted) electrical element
- ◆ Line resistance  $R_{line}$  should keep as small as possible
- ◆  $R_{line} = \frac{l}{A\sigma}$ , where  $\sigma$  is the conductivity
  - large  $\sigma$  means that the layer conducts well (see Fig 3.5)

 


**Figure 3.4** Symbol for a linear resistor



10

### 3.1.1 Interconnect Resistance & Capacitance


- ◆ Designer cannot control  $t$  or  $\sigma$
- ◆  $R_{line} = \frac{l}{A\sigma} = \left(\frac{1}{\sigma t}\right) \cdot \left(\frac{l}{w}\right) = R_s \cdot \left(\frac{l}{w}\right)$
- ◆ If  $l = w$ ,  $R_{line} = R_s = \text{sheet resistance}$ 
  - Unit/per ohms, or ohms per square
  - $R_{line} = R_s * n$ , where  $n = \frac{l}{w}$
- ◆ The line resist depends upon the ratio  $\left(\frac{l}{w}\right)$  of the patterned line

 

**Figure 3.5** Geometry of a conducting line

### 3.1.1 Interconnect Resistance & Capacitance

- ◆ Compute the resistance of a wire

 

**Figure 3.6** Top-view geometry of a patterned line

### 3.1.1 Interconnect Resistance & Capacitance

- ◆ Capacitance: the ability to store electric charge and energy

➤  $C = \frac{Q}{V}$  (1 farad = 1coulomb/volt).

- ◆  $I = C \frac{dV}{dt}$

- ◆ Capacitance exists between any two conducting bodies that electrically separated

- ◆ Parallel-plate formula  $C_{line} = \frac{\epsilon_{ox} w l}{T_{ox}}$ ;  $wl$  is the area;  $\epsilon_{ox}$  is the permittivity of insulating oxide with unit F/cm.

- ◆ Dielectric constant  $\epsilon_{ox} = k\epsilon_0$

➤  $\epsilon_0 = 8.85 \times 10^{-14}$  F/cm

➤  $k = 3.9$  for  $\text{SiO}_2$

➤ low-k dielectrics

 


Figure 3.7 Circuit symbol for a capacitor

 


Figure 3.8 Geometry for calculating the line capacitance

13

high K 低leak , leak都被電容吃掉  
low K 高leak

critical pass用low k

### 3.1.1 Interconnect Resistance & Capacitance

- ◆ Delay (Time constant)

➤ Time constant  $\tau = R_{line} * C_{line}$

➤ If  $V_s(t)$  makes 0->1,  $V(t)$  also rises but is delayed by  $\tau$  and is not as sharp as  $V_s$

➤ VLSI processing are directed toward minimizing both  $R_{line}$  and  $C_{line}$  → fast chip


 


Figure 3.9 Time delay due to the interconnect time constant
 
### 3.1.1 Interconnect Resistance & Capacitance

- ◆ Lumped Element Models
- ◆ Wires are a distributed system
  - Approximate with lumped element models



- ◆ Use single segment  $\pi$ -model for Elmore delay

14: Wires

15

## 3.2 MOSFET

- ◆ What the MOSFET looks like at the physical level
- ◆ An MOSFET is a set of two basic patterned layers
- ◆ Use the concept of **integrated circuit layers** to create a silicon FET

16



## 3.2 MOSFET

- ◆ Recall the circuit symbol for an nFET shown in Figure 3.10(a)
- ◆ We have drawn a simple representation of the nMOS using conducting layers in 3.10(b)
  - The vertical line represents the gate layer and divides another layer into source and drain
- ◆ The gate G is responsible for the absence or presence between S and D.

 


Figure 3.10 nFET circuit symbol and layer equivalents



Figure 3.11 Simplified operational view of an nFET

17

## 3.2 MOSFET

 


Figure 3.12 Layers used to create a MOSFET


 


Figure 3.13 Views of a MOSFET

## 3.2 MOSFET


- ◆ Source and drain are on the same layer and separated by a distance called “channel length”  $L$
- ◆ The width of the drain and source region is called the “channel width”  $W$
- ◆ The aspect ratio of the FET is most important parameter to VLSI designer
  - $\frac{W}{L}$
- ◆ The gate layer is separated by a silicon dioxide (glass) layer acts as an insulator

 

**Figure 3.12** Layers used to create a MOSFET


## 3.2 MOSFET

- ◆ The 3-dimensional structure
- ◆ Silicon dioxide → gate oxide
  - reside directly under the gate
- ◆ nFET and pFET is the same except that the layers used for the drain and source regions
- ◆ nFET has excess # of negatively charged electrons while pFET has positive charges

 


**Figure 3.13** Views of a MOSFET

## Appendix: Fin FET

 

Traditional 2D FET

3D FinFET

 

Conventional Planar FET

### 3.2.1 Electrical Conduction in Silicon

- ◆ Silicon is relative poor conductor (partial conductor)
- ◆ Only a small number of electrons are available to conduct electricity due to thermal excitations
- ◆ An electron gains sufficient energy to break away its atom, it becomes **free** and leaves behind a **hole**

 



Figure 3.14 Creation of electron-hole pairs in silicon


 
## 3.2.1 Electrical Conduction in Silicon



- ◆ The ability of a material to conduct current depends on **the number of free electrons and holes**.
- ◆ Mass-action law:  $np = n_i^2$ 
  - $n$ : the number of free electrons per  $\text{cm}^3$
  - $p$ : the number of free hold per  $\text{cm}^3$
  - $n_i = 1.45 * 10^{10}$ .
- ◆ Pure silicon does not conduct well







### Key

- Electron (  $-q$  )
- Hole (  $+q$  )

**Figure 3.14** Creation of electron-hole pairs in silicon


    
## 3.2.1 Electrical Conduction in Silicon





## 3.2.1 Electrical Conduction in Silicon



### ◆ n-type

- Add donors: arsenic 五價砷 or phosphorus 磷
- Electrons are the majority carriers;  $\mu_n = 1360$  (electron mobility)
- $\sigma_n = q\mu_n n_n$ ;  $n_n$ : doping density of 五價 越大, 電阻越小, 越易導電

### ◆ p-type

- Add acceptor: boron 三價硼
- Holes are majority carriers;  $\mu_p = 480$  (Hole mobility)
- $\sigma_p = q\mu_p n_p$ ;  $n_p$ : doping density of 三價

### ◆ Doping density determines the conductivity in n-type or p-type silicon




25



## 3.2.1 Electrical Conduction in Silicon



### ◆ The pn junction allows conduction in only one direction (diode)

 

**Figure 3.15** Formation and characteristics of a pn junction



26

## 3.2.2 nFETs and pFETs

- ◆ Define the structure of nFET and pFET
- ◆ Several PN junctions; all prevent **unwanted** current flow
- ◆ Choose p-substrate
  - nFET is built directly
  - pFET need n well


 


Figure 3.16 nFET and pFET layers

## 3.2.2 nFETs and pFETs

 

### 3.2.2 nFETs and pFETs


- ◆ n+ heavily doped with donors
- ◆ PN junctions are formed between n+ region and the p type substrate used to block current flow between the substrate and n+ layer
- ◆ p+ section are embedded in an n-type “well” layer.
- ◆ PN junctions all are used to prevent current flow



29

### 3.2.3 Current flow in a FET

- ◆ MOSFETs are voltage controlled switches
- ◆ The creation of conduction layer underneath the gate is due to the capacitance
- ◆ Polycrystal silicon, polysilicon, poly.
- ◆ Oxide capacitance
  - $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$
- ◆ Gate capacitance
  - $C_G = C_{ox} * A_G$
- ◆ Permittivity
  - $\epsilon_{ox} = 3.9 * \epsilon_0$
  - $\epsilon_0 = 8.85 * 10^{-14}$

 


**Figure 3.18** The gate capacitance in an n-channel MOSFET




 
### 3.2.3 Current flow in a FET

- ◆ N-type is physically separated by p-type substrate
- ◆ In (a), no current flow due to PN junction
- ◆ Applying a positive voltage to the gate in (b), induce electrons
- ◆ The formation requires the voltage larger than  $V_{Tn}$



### 3.2.3 Current flow in a FET

- ◆ Driving the current voltage equation
  - The formation requires  $V_{gs} \geq V_{Tn}$
  - Current:  $I_{dn} \cong \mu_n C_{ox} \left(\frac{W}{L}\right) (V_G - V_{Tn}) V_{DS}$ 
    - Electron mobility or surface mobility:  $\mu_n$
  - Device conductance:  $\beta_n = \mu_n C_{ox} \left(\frac{W}{L}\right)$
  - Linear resistance:  $R_n = \frac{1}{\beta_n (V_G - V_{Tn})}$

$$Q = CVol$$

$$Q_c = Cg(V_{gs} - V_{tn})$$

$$I = Qc / t$$


$$t = L / Vel$$

$$I = Cg(V_{gs} - V_{tn}) / (L / Vel)$$

- ◆ pFET behaves in a similar manner except the polarities are reversed

$$\beta_p = \mu_p C_{ox} \left(\frac{W}{L}\right)$$

$$R_p = \frac{1}{\beta_p (V_G - |V_{Tp}|)}$$

 





### 3.2.3 Current flow in a FET



- ◆ MOSFETs are non-linear device in that current  $I$  is a non-linear function of the voltage across it
- ◆ This relationship will be examined in more detail in Chapter 6
- ◆ For simple modeling, however, we often treat the transistor as a linear resistor




33



### 3.2.4 Driving the Gate Capacitance



- ◆ The value of the **capacitance**  $C_G$  determine the amount of charge necessary to charge the voltage, so a large capacitance implies a long delay
  - $Q = C_G V_G$
- ◆ Both the **energy stored in a capacitor** and the **power dissipated** is
 
$$E_e = \frac{1}{2} C_G V_{dd}^2$$
- ◆ Resistors dissipates power by changing it into heat
- ◆ Charge and discharge will be  $2 * E_e = C_G V_{dd}^2$

 

**Figure 3.22** Driving the gate of a FET



34



### 3.2.4 Driving the Gate Capacitance



- ◆ Energy stored in capacitance  $C$  is  $E_e$
- ◆ Energy provided from the  $V_{dd}$  is  $2E_e$
- ◆ Energy loss during the transfer is  $E_e$

$$P = V \left( C \frac{dV}{dt} \right) = \frac{d}{dt} \left( C \frac{V^2}{2} \right)$$

$$E_e = \frac{1}{2} C V_{DD}^2$$



### 3.2.4 Driving the Gate Capacitance



- ◆ Computation causes switching
- ◆ Switching delay are due to the physical characteristics of the devices and interconnect
  - Understand the nature of switching for fast circuit
- ◆ Every switching event requires energy transfer in the circuit
  - This implies that power dissipation





## 3.3 CMOS Layers



- ◆ There are countless variations due to complicated manufacturing process
- ◆ We choose a rather simple process to study
  - n-well process    p當基底
- ◆ We have seen how patterned layers of materials are used to create nFET
- ◆ CMOS fabrication process
  - The sequence of steps that use to take a bare “wafer” of silicon to the finished form of an IC.
- ◆ The n-well process starts with a p-type substrate
  - nFET can be fabricated in the p-type substrate while n-well has to accommodate the pFETs




37



## 3.3 CMOS Layers



- ◆ From this drawing, we can identify the following layer types
  - p-substrate
  - n-well
  - n+ (nFET drain/source)
  - p+ (pFET drain/source)
  - gate oxide
  - gate (polysilicon)

 

**Figure 3.23** MOSFET layers in an n-well process



2024/9/27


38



## 3.3 CMOS Layers



- ◆ Layer implies a region distinct electrical characteristics even though it may be physically at the same geometrical level
- ◆ **FOX: Field OXide (silicon dioxide)** to provide electrical isolation
- ◆ Once base transistor layers are defined, next, we add **conducting** layers

 

**Figure 3.23** MOSFET layers in an n-well process


39




## 3.3 CMOS Layers



- ◆ The top view is shown in Figure 3.24
- ◆ FOX surrounds every transistor so there is an FOX everywhere except at the transistor site
  - Usually not shown explicitly

 

**Figure 3.23** MOSFET layers in an n-well process

 

**Figure 3.24** Top view FET patterning

40





### 3.3 CMOS Layers



#### ◆ Metal interconnect layer

- Modern process allow five or more metal interconnect layers to ease the problem of massive wiring in complex circuits
- Metal layers are **electrically isolated** from each other.
- A hole called **contact cut** is **etched** in the oxide
- Electrical contact requires **contact cuts** and **vias**

metal跟metal叫via  
metal跟substrate叫contact

 


Figure 3.25 Metal interconnect layers

41



### 3.3 CMOS Layers



- ◆ These imply that we can “cross” conducting layers without creating an electrical path between them
- ◆ Metal2 lines can cross over every other layer
  - a via is needed to contact M1

 


Figure 3.26 Interconnect layout example



2024/9/27

Andy Yu-Guang Chen

42



## 3.3 CMOS Layers



### ◆ Metal interconnect layers

- Metal to metal: via
- Metal to the gate: gate contact
- Metal to drain/source: active contact

 


Figure 3.25 Metal interconnect layers

 


Figure 3.26 Interconnect layout example

43



## 3.3 CMOS Layers



### ◆ CMOS digital circuits

- CMOS circuits are designed by creating **nFETs** and **pFETs** in silicon and then **wiring** them together using interconnect lines formed on the conducting layers
- CMOS digital circuits consist **only** transistors and wires
- No other devices are needed, regardless of the complexity of the system


- ◆ Once we learn how to design basic FETs and add the interconnect wiring, then we will understand the basics of CMOS VLSI!



44
 
## 3.4 Designing FET Arrays


- ◆ CMOS logic gates are switching networks that are controlled by the input variables
- ◆ These must be translated into silicon patterns for the final design
- ◆ Let us start with the simplest case of an n-stack where two nFETs are in series
  - Devices can **share** patterned regions to **reduce** layout area or complexity
  - Combine n+ regions
  - Color coding is easier




45

## 3.4 Designing FET Arrays

- ◆ Silicon patterning for series-connected nFETs

 

**Figure 3.27** Silicon patterning for two series-connected nFETs

 

**Figure 3.28** Three series-connected nFETs

46

## 3.4 Designing FET Arrays

- ◆ Parallel-connected FETs can be patterned in the same manner

 


Figure 3.29 Parallel-connected FET patterning

 


Figure 3.30 Alternate layout strategy for parallel FETs

### 3.4.1 Basic Gate Designs


- ◆ For initial stage of crating a CMOS layout design, patterned lines on conducting layers are viewed as paths that “steer” electrical current and establish voltages
  - The widths of the lines are not important at this level
  - Only the topology of the network is needed to trace the logic
  - We are usually more interested in the **signal flow path** and the **circuit topology** than the details of the transistors
- ◆ Some of the important aspects
  - Both the **power supply (VDD)** and **ground (GND)** are routed using metal layer
  - N+ and p+ regions are denoted using the same fill pattern.
    - pFETs are embedded within an n-well boundary.
  - Contacts are needed from metal to n+ or p+ since they are at different levels in the structure

IR drop, VDD離太遠




### 3.4.1 Basic Gate Designs

#### ◆ Translating a NOT gate circuit to silicon

 

**Figure 3.31** Translating a NOT gate circuit to silicon

 


**Figure 3.32** Alternate layout for a NOT gate

能share Vdd or Gnd就share降低area

### 3.4.1 Basic Gate Designs


- ◆ One goal of physical design is to minimize the area of overall chip area
- ◆ Two NOT circuits share the same power supply and ground to reduce area

 


**Figure 3.33** Two NOT gates that share power supply and ground

### 3.4.1 Basic Gate Designs

#### ◆ Non-inverting buffer

 

(a) Logic diagram

 

(b) Layout


**Figure 3.34** Non-inverting buffer

51


### 3.4.1 Basic Gate Designs

#### ◆ Layout of a transmission gate with a driver

##### ➤ Interconnect routing problems

 

(a) Logic diagram

 


(b) Layout

**Figure 3.35** Layout of a transmission gate with a driver

52

### 3.4.1 Basic Gate Designs


#### ◆ NAND2

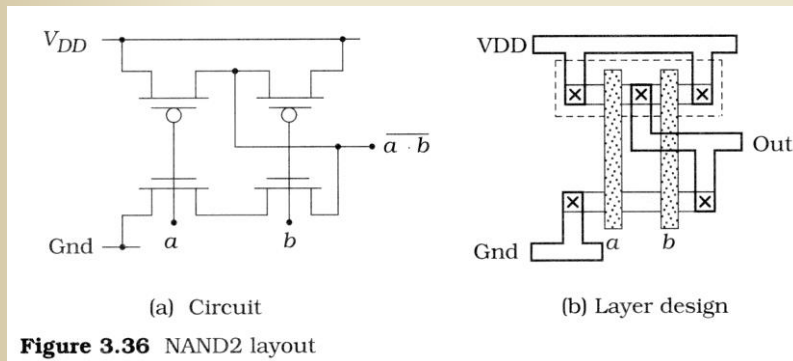

53

### 3.4.1 Basic Gate Designs

#### ◆ NOR2

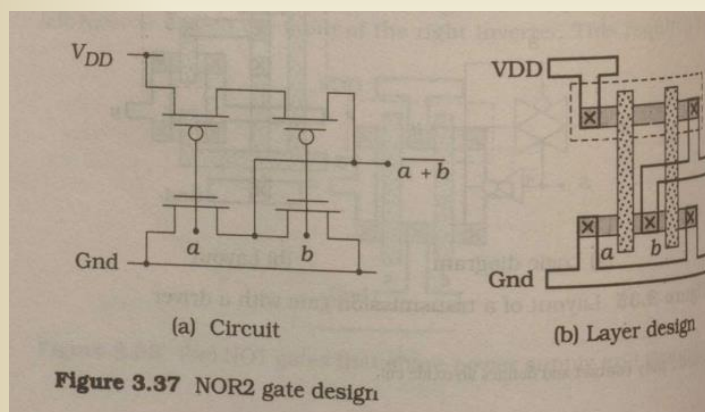


2024/9/27

Andy Yu-Guang Chen

54

### 3.4.1 Basic Gate Designs

#### ◆ NAND2-NOR2 layout comparison

 

2024/9/27

Andy Yu-Guang Chen

55

### 3.4.1 Basic Gate Designs

#### ◆ Layout for 3-input gates


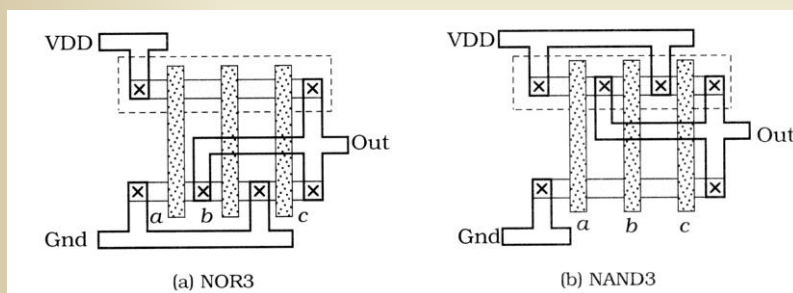


Figure 3.39 Layout for 3-input gates

56

### 3.4.2 Complex Logic Gates

- ◆ Consider the circuit that implements the function  $f = \overline{a + b \cdot c}$

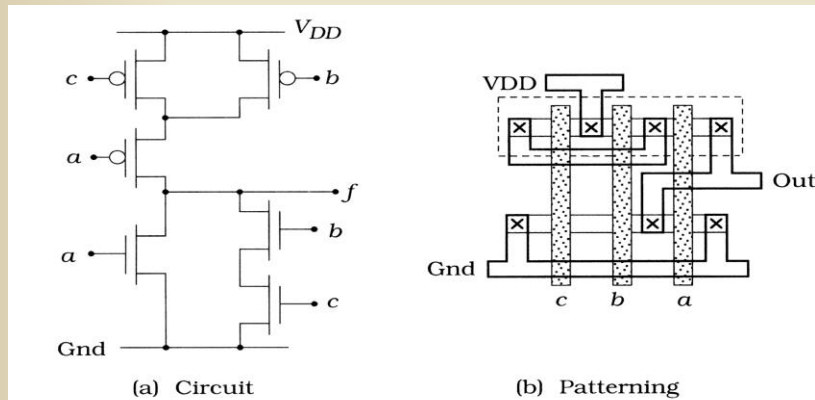

**Figure 3.40** Extension of layout technique to a complex logic gate


2024/9/27

Andy Yu-Guang Chen

57

### 3.4.2 Complex Logic Gates

- ◆ Suppose that we flip the metal wiring pattern around an imaginary horizontal line
- ◆ Tracing out the circuit yields the schematic in Figure 3.41(b)
  - $g = \overline{a \cdot (b + c)}$
  - Logical dual of  $f$

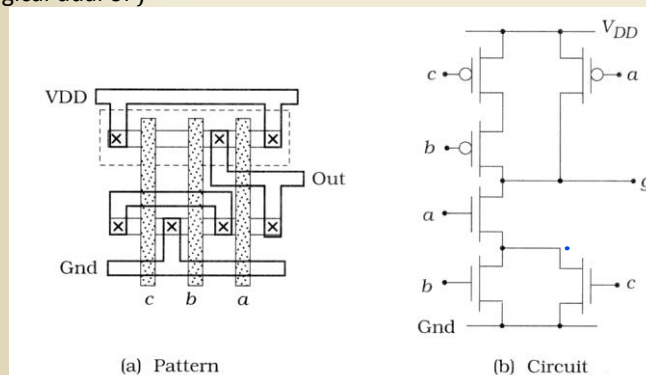

**Figure 3.41** Creation of the dual network


2024/9/27

Andy Yu-Guang Chen

58

### 3.4.2 Complex Logic Gates

◆ General AOI expression  $F = \overline{x \cdot y + z \cdot w}$

 

**Figure 3.42** A general 4-input AOI gate

2024/9/27

Andy ru-Guang Chen


59

### 3.4.3 General Discussion

- ◆ It is possible to share n+ and p+ regions to reduce area
  - This is not always possible, especially in complicated arrangements
- ◆ Regular patterns yields the best packing density
- ◆ Every gate requires a VDD and VSS which runs into horizontal metal lines

### 3.4.3 General Discussion

#### ◆ General gate layout geometry

 

**Figure 3.43** General gate layout geometry

2024/9/27

Andy Yu-Guang Chen

61

### 3.4.3 General Discussion

#### ◆ Simple **stick diagrams**

- Each layer is represented by a distinct color
  - the drawing can be monochrome and layers have been represented by different line features such as varying the linewidth or using a dashed line
- The routing consists of colored lines that obey the rules of chip formation

#### ◆ Most commonly used colors

- Polysilicon (gates): Red
- Doped n+/p+ (active): Green
- N-Well: Yellow (varies)
- Metal 1: Blue
- Metal2: Grey (varies)
- Contacts: Black X's

2024/9/27

Andy Yu-Guang Chen

62






### 3.4.3 General Discussion



#### ◆ Basic stick layout diagram

 

2024/9/27

Andy Yu-Guang Chen

63



### 3.4.3 General Discussion



#### ◆ Rules

- A red line crossing a green line creates a transistor
- Red over green inside a yellow border region is a pFET; otherwise it is an nFET
- Red may cross blue or grey
- Blue may cross red, green, or gray
- Grey may cross red, green, or blue
- Transistor contacts must be placed from blue to green
- Vias must be specified to contact blue to grey
- A (poly) contact must be used to connect blue to red



2024/9/27


Andy Yu-Guang Chen

64


 
### 3.4.3 General Discussion

- ◆ A more structured technique is to apply graph theory
  - Using graph element to represent a FET




2024/9/27

Andy Yu-Guang Chen

65
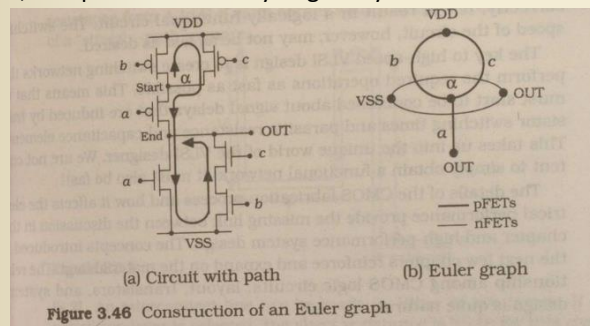
### 3.4.3 General Discussion

- ◆ Euler graphs aid in the placement and wiring of circuits when transistors have shared drain/source regions
- ◆ Eulerian path
  - The path starts at the vertex shown and follows the arrow to the end vertex, and passes over every edge only once




2024/9/27

Andy Yu-Guang Chen

66

### 3.4.3 General Discussion

#### ◆ Layout using an Euler graph

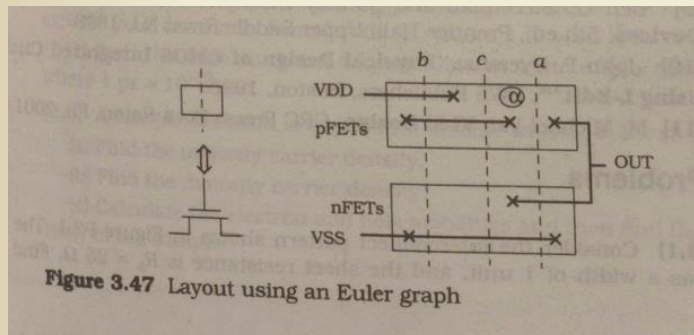

2024/9/27

Andy Yu-Guang Chen

67

## Summary

- ◆ In this chapter we have seen the basics of translating FET logic circuits to silicon
- ◆ The layout considerations presented here are sufficient to create complex logic networks using a set of standard MOSFETs as building blocks
- ◆ In many designs it is possible to simply place reasonably sized transistors as specified by the layout, and wire them together
- ◆ The key to high-speed VLSI design is to create switching network perform the required operations as fast as possible
- ◆ This takes us into the unique world of the VLSI designer. We are not content to simply obtain a functional network: it must also be fast!
- ◆ The concepts introduced the next few chapters reinforce and expand on the material here



2024/9/27

Andy Yu-Guang Chen

68




# Q&A




Andy Yu-Guang Chen

Slide 69







**Andy, Yu-Guang Chen**  
 Assistant Professor, Department of EE, NCU  
 Email: [andyygchen@ee.ncu.edu.tw](mailto:andyygchen@ee.ncu.edu.tw)  
 FB: Yu-Guang Chen  
 IG: ncu.eda.andy  
 Google account: andyygchen.ncu



2024/9/27

Andy Yu-Guang Chen

70